



Applied Physics (NS-1001)

Quiz # 5A

Fall 2025

Instructor: Dr. Tashfeen Zehra

Name:


Roll #:

Section: BCS-A

CLO3

Date: 01-12-2025

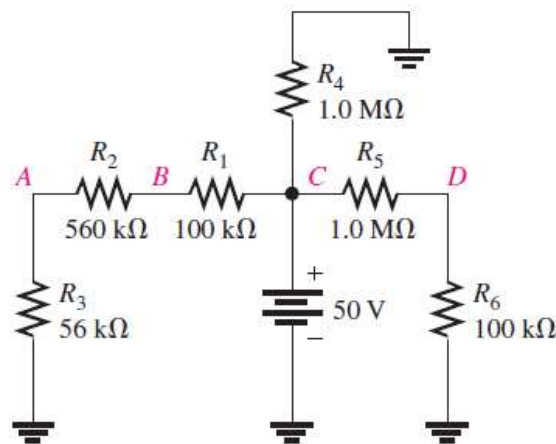**Q.1:** Determine the resistance of the circuit in Figure 1 as seen from the voltage source. (7M)



### Step 1: Calculate the total resistance of each parallel branch

The circuit has three parallel branches.

- Branch 1:  $R_1$ ,  $R_2$ ,  $R_3$  in series with values  $R_1 = 100 \text{ k}\Omega$ ,  $R_2 = 560 \text{ k}\Omega$ ,  $R_3 = 56 \text{ k}\Omega$ .
- Branch 2:  $R_5$ ,  $R_6$  in series with values  $R_5 = 1 \text{ M}\Omega$ ,  $R_6 = 100 \text{ k}\Omega$ .
- Branch 3: A single resistor  $R_4$  with value  $R_4 = 1 \text{ M}\Omega$ .

The total resistance of each branch is:

- $R_{\text{Branch1}} = R_1 + R_2 + R_3 = 100 \text{ k}\Omega + 560 \text{ k}\Omega + 56 \text{ k}\Omega = 716 \text{ k}\Omega$ .
- $R_{\text{Branch2}} = R_5 + R_6 = 1 \text{ M}\Omega + 100 \text{ k}\Omega = 1000 \text{ k}\Omega + 100 \text{ k}\Omega = 1100 \text{ k}\Omega$ .
- $R_{\text{Branch3}} = R_4 = 1 \text{ M}\Omega = 1000 \text{ k}\Omega$ .

## Step 2: Calculate the total equivalent resistance of the parallel circuit

The total equivalent resistance ( $R_{eq}$ ) for the three parallel branches is calculated using the formula for parallel resistors:

$$\frac{1}{R_{eq}} = \frac{1}{R_{\text{Branch1}}} + \frac{1}{R_{\text{Branch2}}} + \frac{1}{R_{\text{Branch3}}}$$

$$\frac{1}{R_{eq}} = \frac{1}{716 \text{ k}\Omega} + \frac{1}{1100 \text{ k}\Omega} + \frac{1}{1000 \text{ k}\Omega}$$

$$\frac{1}{R_{eq}} \approx 0.0013966 \text{ k}\Omega^{-1} + 0.0009091 \text{ k}\Omega^{-1} + 0.001 \text{ k}\Omega^{-1}$$

$$\frac{1}{R_{eq}} \approx 0.0033057 \text{ k}\Omega^{-1}$$

$$R_{eq} \approx \frac{1}{0.0033057 \text{ k}\Omega^{-1}} \approx 302.5 \text{ k}\Omega$$